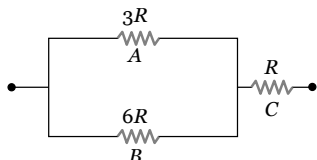


Heating and Chemical Effect of Current

SET Self Evaluation Test - 20

- An electric kettle has two coils. When one of these is switched on, the water in the kettle boils in 6 minutes. When the other coil is switched on, the water boils in 3 minutes. If the two coils are connected in series, the time taken to boil the water in the kettle is
 - 3 minutes
 - 6 minutes
 - 2 minutes
 - 9 minutes
- A 3° rise in temperature is observed in a conductor by passing a certain current. When the current is doubled, the rise in temperature will be
 - $15^\circ C$
 - $12^\circ C$
 - $9^\circ C$
 - $3^\circ C$
- Two identical electric lamps marked 500 W, 220 V are connected in series and then joined to a 110 V line. The power consumed by each lamp is
 - $\frac{125}{4} W$
 - $\frac{25}{4} W$
 - $\frac{225}{4} W$
 - 125 W
- When 1 gm hydrogen ($e.c.e. = 1.044 \times 10^{-8} kg / C$) forms water, 34 kcal heat is liberated. The minimum voltage required to decompose water is
 - 0.75 V
 - 3 V
 - 1.5 V
 - 4.5 V
- In how much time, one litre of H_2 will be collected by 5 A current ? (If $Z = 1 \times 10^{-8} kg / C$ and density of $H_2 = 0.09 kg / m^3$)
 - 30 minutes
 - 15 minutes
 - 45 minutes
 - 60 minutes
- The three resistances A, B and C have values 3R, 6R and R respectively. When some potential difference is applied across the network, the thermal powers dissipated by A, B and C are in the ratio
 - 2 : 3 : 4
 - 2 : 4 : 3
 - 4 : 2 : 3
 - 3 : 2 : 4
- If the length of the filament of a heater is reduced by 10%, the power of the heater will
 - Increase by about 9%
 - Increase by about 11%
 - Increase by about 19%
 - Decrease by about 10%
- A thermo couple develops $40 \mu V / kelvin$. If hot and cold junctions be at $40^\circ C$ and $20^\circ C$ respectively then the emf



develops by a thermopile using such 150 thermo couples in series shall be

- $150 mV$
 - $80 mV$
 - $144 mV$
 - $120 mV$
- Amount of electricity required to pass through the H_2O voltmeter so as to liberate 11.2 litre of hydrogen will be
 - 1 Faraday
 - $\frac{1}{2}$ Faraday
 - 2 Faraday
 - 3 Faraday
 - The resistance of the filament of a lamp increases with the increase in temperature. A lamp rated 100 W, 220 V is connected across 220 V power supply. If the voltage drops by 10% then the power of lamp will be
 - 90 W
 - 81 W
 - Between 90 W and 100 W
 - Between 81 W and 90 W
 - In the following circuit, 18Ω resistor develops 2 J/sec due to current flowing through it. The power developed across 10Ω resistance is
 - 125 W
 - 10 W
 - $\frac{4}{5} W$
 - 25 W
-
- If resistance of the filament increases with temperature, what will be power dissipated in a 220 V- 100 W lamp when connected to 110 V power supply
 - 25 W
 - < 25 W
 - > 25 W
 - None of these
 - Total surface area of a cathode is $0.05 m^2$ and 1 A current passes through it for 1 hour. Thickness of nickle deposited on the cathode is (Given that density of nickle = $9 gm / cc$ and it's E.C.E. = $3.04 \times 10^{-4} gm / C$)
 - 2.4 m
 - $2.4 \mu m$
 - $2.4 \mu m$
 - None of these
 - Two bulbs consume same power when operated at 200 V and 300 V respectively. When these bulbs are connected in series across a D.C. source of 500 V, then
 - Ratio of potential difference across them is 3/2
 - Ratio of potential difference across them is 9/4
 - Ratio of power consumed across them is 4/9
 - Ratio of power consumed across them is 2/3

AS Answers and Solutions

(SET -20)

1. (d) In series $\frac{1}{P_s} = \frac{1}{P_1} + \frac{1}{P_2}$

$$\Rightarrow \frac{1}{(H_s / t_s)} = \frac{1}{(H_1 / t_1)} + \frac{1}{(H_2 / t_2)}$$

$$\therefore H_s = H_1 = H_2 \text{ So } t_s = t_1 + t_2 = 6 + 3 = 9 \text{ min}$$


2. (b) $i^2 R t = C \theta = 3C$; C = Thermal capacity

$$\text{when } i_1 = 2i \Rightarrow C \theta_1 = 4i^2 R t = 4 \times 3C \Rightarrow \theta_1 = 12^\circ C$$

3. (a) Voltage across each bulb $V' = \frac{110}{2} = 55 \text{ V}$ so, power consumed by each bulb will be

$$P' = \left(\frac{55}{220}\right)^2 \times 500$$

$$= \frac{125}{4} \text{ W}$$

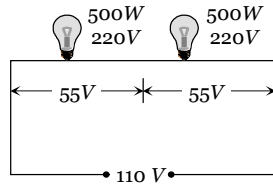

4. (c) $m = Zit \Rightarrow it = \frac{m}{Z} = \frac{1 \times 10^{-3}}{1.044 \times 10^{-8}} C = \frac{10^5}{1.044} C$

$$\text{Given } H = 34 \text{ kcal} = 4.2 \times 34 \times 10^3 \text{ J}$$

$$\Rightarrow \text{Heat generated } H = Vit = V \cdot \frac{10^5}{1.044}$$

$$\Rightarrow V = \frac{4.2 \times 34 \times 1.044}{10^2} = 4.2 \times 0.34 \times 1.044 = 1.5 \text{ V}$$

5. (a) $m = zit \Rightarrow 10^{-3} \times 0.09 = 1 \times 10^{-8} \times 5 \times t \Rightarrow t = 30 \text{ min}$


6. (c) Thermal power in $A = P_A = \left(\frac{2i}{3}\right)^2 3R = \frac{4}{3} i^2 R$

$$\text{Thermal power in } B = P_B = \left(\frac{i}{3}\right)^2 6R = \frac{2}{3} i^2 R$$

Thermal power in

$$C = P_C = i^2 R$$
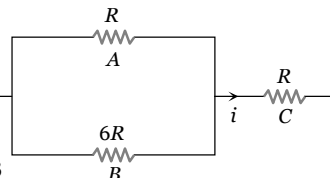
$$\Rightarrow P_A : P_B : P_C = \frac{4}{3} : \frac{2}{3} : 1 = 4 : 2 : 3$$



7. (b) $P \propto \frac{1}{R}$ and $R \propto l \Rightarrow P \propto \frac{1}{l}$

$$\Rightarrow \frac{P_1}{P_2} = \frac{l_2}{l_1} \Rightarrow \frac{P_1}{P_2} = \frac{(100 - 10)}{100} = \frac{90}{100} \Rightarrow P_2 = 1.11 P_1$$

$$\% \text{ change in power} = \frac{P_2 - P_1}{P_1} \times 100 = 11\%$$

8. (d) The temperature difference is $20^\circ C = 20 \text{ K}$. So that thermo emf developed

$$E = \alpha \theta = 40 \frac{\mu V}{K} \times 20 K = 800 \mu V$$

$$\text{Hence total emf} = 150 \times 800 = 12 \times 10^4 \mu V = 120 \text{ mV}$$

9. (a) 22.4 litre $H_2 = 1$ mole of $H_2 = N$ molecules of H_2 ***
 $= 2N$ atoms of H .

So charge required to liberate 22.4 litre of $H_2 = 2Ne = 2F$.

Hence charge required to liberate 11.2 litre of $H_2 = F$.

10. (d) Let the resistance of the lamp filament be R . Then $100 = \frac{(220)^2}{R}$. When then voltage drops, expected

power is $P = \frac{(220 \times 0.9)^2}{R'}$. Here R' will be less than R , because now the rise in temperature will be less.

Therefore P is more than $\frac{(220 \times 0.9)^2}{R} = 81 \text{ W}$


But it will not be 90% of earlier value, because fall in temperature is small. Hence (d) is correct.

11. (b) The given circuit can be redrawn as follows

$$\frac{i_1}{i_2} = \frac{9}{18} = \frac{1}{2}$$

$$\text{and } i = i_1 + i_2$$
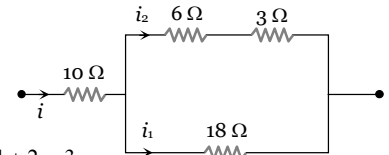
$$\Rightarrow \frac{i}{i_1} = 1 + \frac{i_2}{i_1} = 1 + 2 = 3$$



$$\text{From } P = i^2 R \Rightarrow \frac{P_{10\Omega}}{P_{18\Omega}} = \left(\frac{i}{i_1}\right)^2 \times \frac{10}{18} \Rightarrow P_{10\Omega} = 10 \text{ W}$$

12. (c) If resistance does not vary with temperature P

consumed $= \left(\frac{V_A}{V_R}\right)^2 \times P_R = \left(\frac{110}{220}\right)^2 \times 100 = 25 \text{ W}$. But in second cases resistance decreases so consumed power will be more than 25 W

13. (c) Mass deposited = density \times volume of the metal

$$m = \rho \times A \times X \quad \dots (i)$$

Hence from Faraday's first law $m = Zit \dots (ii)$

So from equation (i) and (ii)

$$Zit = \rho \times Ax \Rightarrow x = \frac{Zit}{\rho A}$$

$$= \frac{3.04 \times 10^{-4} \times 10^{-3} \times 1 \times 3600}{9000 \times 0.05} = 2.4 \times 10^{-6} \text{ m} = 2.4 \mu \text{m}$$

14. (c) $P = \frac{V^2}{R} \therefore R = \frac{V^2}{P}$ or $R \propto V^2$ i.e. $\frac{R_1}{R_2} = \left(\frac{200}{300}\right)^2 = \frac{4}{9}$

When connected in series potential drop and power consumed are in the ratio of their resistances. So,

$$\frac{P_1}{P_2} = \frac{V_1}{V_2} = \frac{R_1}{R_2} = \frac{4}{9}$$